



Phys219_2017 - Ryan Kaufmann/Exp. 2 (LCR Resonance Circuit)/Prelab assignment for Exp2

SIGNED by Ryan Kaufmann Oct 02, 2017 @10:42 AM PDT

Ryan Kaufmann Oct 02, 2017 @09:06 AM PDT

Experiment 2: Pre-Lab


Ryan Kaufmann Oct 02, 2017 @09:07 AM PDT

Questions 1:

Ryan Kaufmann Oct 02, 2017 @09:09 AM PDT

Consider the circuit of Fig. 1. What are γ and ω_0 with in units of inverse seconds?

Ryan Kaufmann Oct 02, 2017 @09:23 AM PDT

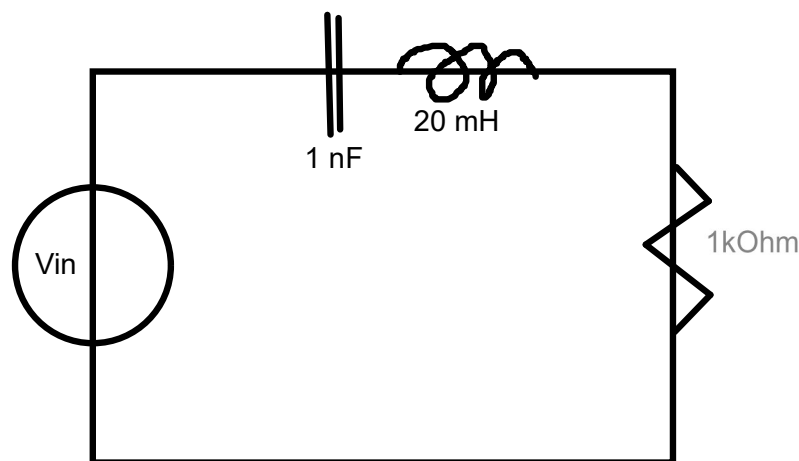

Ryan Kaufmann Oct 02, 2017 @09:21 AM PDT

We can use the equations given to find the γ and ω_0 of the given figure. Thus we get the following:

Ryan Kaufmann Oct 02, 2017 @09:30 AM PDT

$$\gamma = \frac{R}{L} = \frac{1000}{0.020} \text{ Hz} = 50 \cdot 10^3 \text{ Hz}$$

Ryan Kaufmann Oct 02, 2017 @09:30 AM PDT

Question 2:

Ryan Kaufmann Oct 02, 2017 @09:32 AM PDT

Assume V_0 and V_{in} in equations 1 and 4 are both +1V. Use the above values of γ and ω_0 to make plots of equations 1 and 4 with units on the x and y axes. Modify the python script Plotfunction.py for this purpose.

Ryan Kaufmann Oct 02, 2017 @09:37 AM PDT

Plugging in our values for γ and ω_0 gives us the following equations:

Processing math: 0%

Ryan Kaufmann Oct 02, 2017 @10:09 AM PDT

$$V_r(t) = \frac{\gamma}{\omega_0} e^{\frac{-t}{\gamma}} \cos(\omega_0 t + \phi_0) \quad V_r(t) = \frac{50 \cdot 10^3}{224 \cdot 10^3} e^{\frac{-50 \cdot 10^3 t}{2}} \cos(224 \cdot 10^3 t + \frac{\pi}{2})$$


$$V_r(t) = 0.2232 e^{-25000 t} \cos(224000 t + \frac{\pi}{2})$$

$$V_r(\omega) = \frac{1}{\sqrt{1 + (\frac{1}{\gamma \omega})^2 (\omega^2 - \omega_0^2)^2}} \quad V_r(\omega) = \frac{1}{\sqrt{1 + (\frac{1}{50000 \omega})^2 (\omega^2 - 224000^2)^2}}$$

Ryan Kaufmann Oct 02, 2017 @10:09 AM PDT


And the following graphs:

Ryan Kaufmann Oct 02, 2017 @10:36 AM PDT

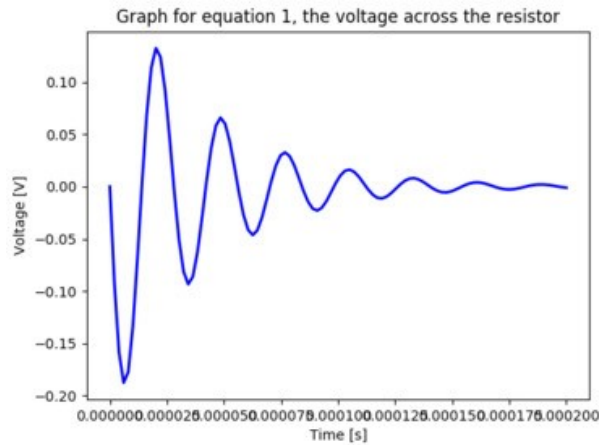

PrelabEquation1.png(31.7 KB)

Ryan Kaufmann Oct 02, 2017 @10:36 AM PDT

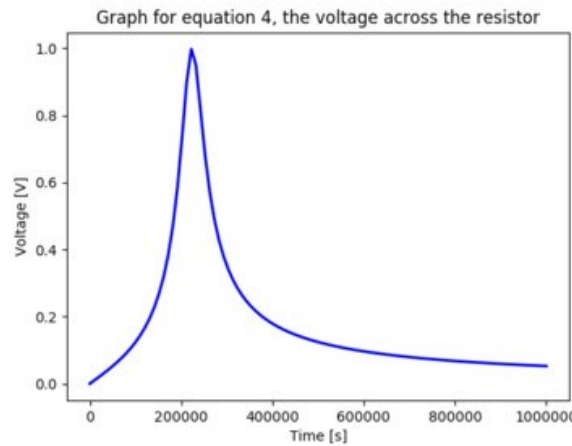

PrelabEquation4.png(25.8 KB)

Ryan Kaufmann Oct 02, 2017 @09:34 AM PDT

Question 3:

Ryan Kaufmann Oct 02, 2017 @09:35 AM PDT

In section 4.1, estimate the period of the square wave you need to observe 10 oscillations in $V_r(t)$.

Ryan Kaufmann Oct 02, 2017 @10:38 AM PDT

We can take our number for ω_0 and use it to calculate the period for 10 oscillations in $V_r(t)$. This calculation is as follows:

Ryan Kaufmann Oct 02, 2017 @10:42 AM PDT

$$\omega_0 = 224000 \text{ Hz} = 2\pi f \quad f = \frac{224000}{2\pi} \text{ Hz} = 35650.7 \text{ Hz} \quad T_1 = \frac{1}{f} = 0.00002805 \text{ seconds} \quad T_{10} = 10 \cdot T_1 = 0.0002805 \text{ seconds}$$