



## Phys219\_2017 - Ryan Kaufmann/Exp. 3 (Diodes and Transistors)/Prelab assignment for Exp 3

SIGNED by Ryan Kaufmann Oct 23, 2017 @10:35 AM PDT

Ryan Kaufmann Oct 23, 2017 @12:33 AM PDT

# Experiment 3: Semiconductor Diodes and Transistors

Partner: Eric Brock


Ryan Kaufmann Oct 23, 2017 @12:33 AM PDT

## 3.1 Prelab Exercise

Ryan Kaufmann Oct 23, 2017 @12:35 AM PDT

To start, we made a plot for the I-V curve of a diode using certain parameters. We assumed that  $I_0$  was 10 microamperes, and  $T$  was 300 Kelvin. We then plotted the function over -0.3V to 0.3V. The Plotfunction.py script gave us the following graph:

Ryan Kaufmann Oct 23, 2017 @12:35 AM PDT

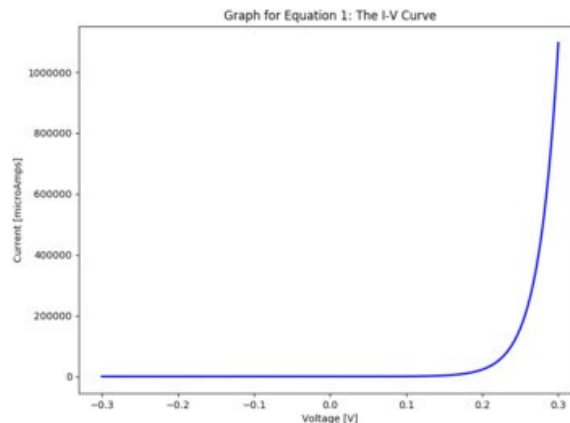

Prelab1-VCurve.png(27.7 KB)

Ryan Kaufmann Oct 23, 2017 @12:37 AM PDT

Using the same pretend diode, we also looked at a solution where we had measured the voltage drop over the resistor and the input voltage into the diode. Using these two values we could get the voltage drop across the diode as well as the current running through the diode. We calculated the following:

Ryan Kaufmann Oct 23, 2017 @12:40 AM PDT

$$V_r = +1.8V$$

$$V_{in} = +2.0V$$


$$V_d = V_{in} - V_r = 2.0V - 1.8V = +0.2V$$

$$I(V_d) = I_0(e^{\frac{V_d}{T \cdot k_B}} - 1) = 10(e^{\frac{0.2}{300 \cdot 8.617 \cdot 10^{-5}}} - 1)\mu A = 22.898mA$$

Ryan Kaufmann Oct 23, 2017 @10:35 AM PDT

In the last part of the prelab, we want to make a circuit that provides a DC offset so that the base-emitter junction is forward biased even if the input signal has no DC component. In order to do this, we will take advantage of the  $V_{cc}$  input, which is typically a constant voltage. We can use this to provide a base voltage as our  $V_b$ , by providing a resistance branch to connect to  $V_b$  in the transistor, giving us the following diagram for a fixed base bias:

Ryan Kaufmann Oct 23, 2017 @10:35 AM PDT

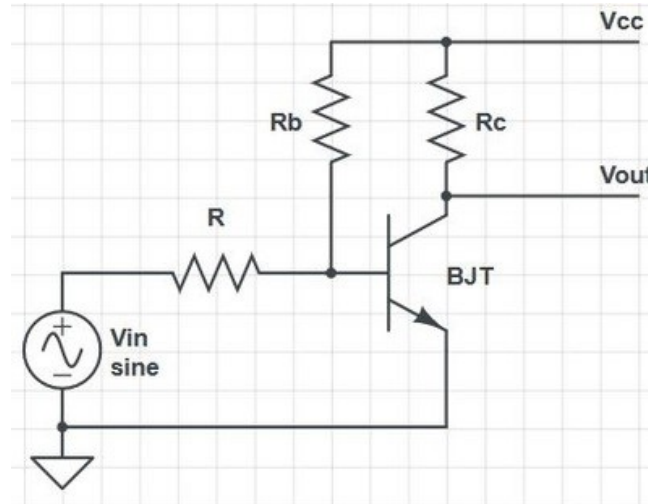

CircuitDiagram.JPG(36.9 KB)